

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
THIRD SEMESTER B.TECH DEGREE EXAMINATION, APRIL 2018

Course Code: CS203

Course Name: SWITCHING THEORY AND LOGIC DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 3 marks

Marks

- | | | |
|---|---|-----|
| 1 | Perform the following operations: | (3) |
| | i) $(E39)_{16} + (3F9)_{16}$ ii) $(721)_8 - (32)_8$ | |
| | iii) BCD addition of 0110 0111 and 0101 0011 | |
| 2 | Perform the following conversions: (Show the steps of conversion) | (3) |
| | i) $(463.25)_{10}$ to binary ii) $(36.25)_{10}$ to octal iii) $(AF9.0C)_{16}$ to binary | |
| 3 | Using Boolean postulates simplify the following expressions: | (3) |
| | i) $x+x'y$ ii) $xy+x'z+yz$ iii) $x'y'z+x'yz+xy'$ | |
| 4 | Express the following functions: | (3) |
| | i) $F_1=AB+B'C$ in sum of Minterms form. | |
| | ii) $F_2=A+B'C$ in product of Maxterms form. | |

PART B

Answer any two full questions, each carries 9 marks

- | | | |
|---|---|-----|
| 5 | Perform subtraction of the following using r's complement and (r-1)'s complement methods: | (9) |
| | i) $(7235)_{10} - (346)_{10}$ ii) $(1000100)_2 - (1110100)_2$ | |
| 6 | Given $F(A, B, C, D) = \sum(1, 4, 6, 7, 8, 9, 10, 11, 15)$. Simplify using Quin-McClusky method and determine the prime implicants, essential prime implicants and the minimized Boolean expression. | (9) |
| 7 | a) Using K-map, simplify the Boolean function F in sum of products form, using the don't care conditions d: | (5) |
| | $F(w, x, y, z) = w'(x'y + x'y' + xyz) + x'z'(y+w)$ | |
| | $d(w, x, y, z) = w'x(y'z + yz') + wyz$ | |
| | b) Give the IEEE Single precision format for floating point number representation with explanation. Determine the floating-point binary number represented by the following single precision floating point representation. | (4) |

"1100 1010 1100 0111 0001 0000 0011 1011"

PART C

Answer all questions, each carries 3 marks

- | | | |
|----|--|-----|
| 8 | Implement $F = A(B+CD) + B'C$ with NAND gates. | (3) |
| 9 | Derive the simplified Boolean output functions of a full subtractor. | (3) |
| 10 | Explain the terms: | (3) |
| | i) Race-around condition ii) Edge triggering of flip-flops | |

- 11 Implement D flip-flop using NAND gates and explain its working. (3)

PART D

Answer any two full questions, each carries 9 marks

- 12 a) Implement a 4-bit magnitude comparator. Give a Boolean function to check the equality relation of a pair of bits and derive logic functions for the outputs of the magnitude comparator. (5)
- b) Give the characteristic table and excitation table of RS flip-flop and JK flip flop. (4)
- 13 a) Implement the function with a multiplexer: $F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$ (5)
- b) Explain state table and state diagram with an example. (4)
- 14 a) What is a Master-slave flip-flop? Explain its working with a timing diagram. (4)
- b) How can the principle of look-ahead carry reduce the carry propagation time in a binary parallel adder? Derive the Boolean functions for the carry outputs at different stages of a look-ahead carry generator. (6)

PART E

Answer any four full questions, each carries 10 marks

- 15 Design a BCD ripple counter. Also verify its operation by means of a timing diagram. (10)
- 16 a) Explain PLA with a block diagram. (4)
- b) Design a counter that has a repeated sequence of the following six states: 000, 001, 010, 100, 101, 110 (6)
- 17 a) Explain the various types of ROMs (4)
- b) Implement a 4-bit bidirectional shift register with parallel load. (6)
- 18 a) Sketch the block diagram of a BCD adder. Using a truth table derive the condition for correction in BCD addition. (5)
- b) Design a serial adder using a full adder and shift registers. (5)
- 19 a) Explain the construction of a 32 X 4 ROM with a logic diagram. (5)
- b) Give the logical configuration of shift registers. With a block diagram, explain the use of shift registers for serial transfer of data. (5)
- 20 Draw a flow chart and explain the addition/ subtraction of two binary numbers in signed magnitude representation. (10)
