

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018

**Course Code: CS203**

**Course Name: SWITCHING THEORY AND LOGIC DESIGN (CS)**

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions, each carries 3 marks.*

- |  | Marks |
|--|-------|
| 1 Find the 9's and 10's complement of $(24579.12)_{10}$ .                        | (3)   |
| 2 Convert $(455)_{10}$ to base-4,8 and 16.                                       | (3)   |
| 3 Express the following functions as product of max-terms:                       | (3)   |
| a) $F(X,Y,Z) = Y' + XZ' + XY'Z'$ b) $F(A,B,C) = C(A+B')(A'+B'+C')$               |       |
| 4 Use Boolean Algebra to show that $A'BC' + AB'C' + AB'C + ABC' + ABC = A + BC'$ | (3)   |

**PART B**


*Answer any two full questions, each carries 9 marks.*

- |   |     |
|---|-----|
| 5 Simplify $F(A,B,C,D) = \Sigma(1,4,6,7,8,9,10,11,15)$ using Tabulation method and determine the prime implicants, essential prime implicants and the minimized Boolean expression. | (9) |
| 6 a) Subtract $(9F2C)_{16}$ from $(A96B)_{16}$ using 15's and 16's complement method.   | (4) |
| b) Subtract 366 from 170 in BCD using 10's complement addition.   | (3) |
| c) Perform $(417)_8 - (232)_8$ using 8's complement addition.   | (2) |
| 7 a) Using K-map simplify the Boolean function F as Sum of Products using the don't care conditions d.  | (4) |
| $F(w,x,y,z) = w'(x'y + x'y' + xyz) + x'z'(y+w)$   |     |
| $d(w,x,y,z) = w'x(y'z + yz) + wyz$  |     |
| b) Represent the following decimal numbers in signed 2's complement 8-bit numbers: i) +43    ii) -19  | (3) |
| c) Convert the decimal number $3.248 \times 10^{-4}$ to IEEE 754 standard single precision floating point binary number.  | (2) |

**PART C**

*Answer all questions, each carries 3 marks.*

- |   |     |
|---|-----|
| 8 Differentiate combinational and sequential circuits.  | (3) |
| 9 Given the block diagram of half-subtractor, implement a full-subtractor using half-subtractors.         | (3) |
| 10 Write the excitation tables of SR, JK and T flip-flops.  | (3) |
| 11 Given below is a sequential circuit using D flip-flop. Write the state table and draw a state diagram. | (3) |

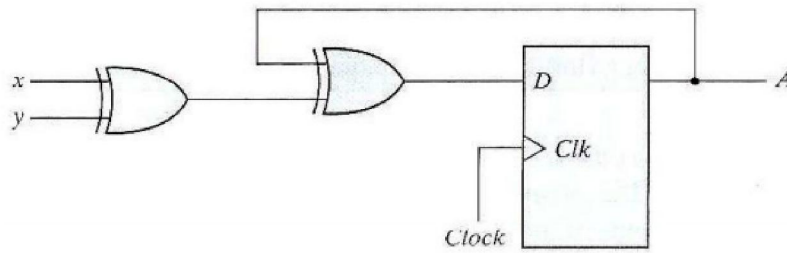**PART D**

*Answer any two full questions, each carries 9 marks.*

- 12 a) Design a sequential circuit with JK Flip flops to satisfy the following state equation. (5)  
 $A(t+1)=A'B'CD + A'B'C + ACD + AC'D'$      $B(t+1)= A'C + CD' + A'BC'$   
 $C(t+1)= B$      $D(t+1)=D'$
- b) Design and implement a decoder that decodes BCD digits (0000 to 1001). (4)
- 13 a) Design and implement a 2-bit magnitude comparator using 4X16 decoder. (5)
- b) Implement  $f(A,B,C,D)= \Sigma(0,2,3,6,8,9,13,14)$  using 8 x 1 MUX . (4)
- 14 What is race around condition? Why does it occur? Discuss how master-slave flip-flop eliminates it. (9)

**PART E**

*Answer any four full questions, each carries 10 marks.*

- 15 a) Draw the logic diagram of a 4-bit Johnson counter and explain the working with a timing diagram. (8)
- b) Compare Ring counter and Johnson counter. (2)
- 16 a) Explain the working of 3-bit *Universal* Shift Register. (8)
- b) Give 2 applications of shift register. (2)
- 17 a) Design a combinational circuit using ROM that accepts a 3-bit binary number and generates output equal to the square of the input number. Use decoder of suitable size to implement ROM. (7)
- b) What size of ROM would it take to implement (3)
- A BCD adder/subtractor with a control input to select between the addition and subtraction.
  - A binary multiplier that multiplies two 4-bit numbers.
  - Dual 4-line to 1-line multiplexers with common selection inputs.
- 18 Design a synchronous counter using JK flip-flops to count the sequence 0,5,6,7,3,2 and then repeats. (10)
- 19 a) Compare static and dynamic RAMs. (3)
- b) A combinational circuit is defined by the functions: (7)  
 $F1(A,B,C)=\Sigma(3,5,6,7)$      $F2= \Sigma(0,2,4,7)$   
 Implement the circuit with a PLA having 3 inputs, four product terms and 2 outputs.
- 20 With the help of a flowchart explain the addition/subtraction of binary numbers in sign magnitude form. (10)

\*\*\*\*