

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree (S,FE) Examination January 2022 (2015 Scheme)

Course Code: CS203**Course Name: SWITCHING THEORY AND LOGIC DESIGN**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer all questions, each carries 3 marks.*

Marks

- 1 Convert the following numbers from the given base to the bases indicated (3)
- a) $(153.87)_{10}$ to Hexadecimal
- b) $(127)_8$ to Decimal
- c) $(11101.1001)_2$ to Octal
- 2 Differentiate digital systems and analogue systems. (3)
- 3 Represent +51 and -51 in 1's complement and 2's complement form (3)
- 4 Convert the following expression into sum of product and product of sum (3)
- $(AB + C)(B + C'D)$

PART B*Answer any two full questions, each carries 9 marks.*

- 5 a) Represent the number 85.125 using the double-precision floating point format (5)
- IEEE-754 standard.
- b) Find Subtraction of 1B06 and 77C using 15's complement method (4)
- 6 Simplify the following expressions using K-Map, and implement it with two-level NAND gate circuits: (9)
- $AB' + ABD + ABD' + A'C'D' + A'BC'$
- 7 Use tabulation method to identify the simplified Boolean expression for the (9)
- function, $F(A,B,C,D) = \sum m(0,1,2,3,5,7,8,10,12,13,15)$

PART C*Answer all questions, each carries 3 marks.*

- 8 Give the design and circuit for a half adder (3)
- 9 Implement the function $F(A, B, C, D) = \sum (0, 1, 3, 5, 7, 10, 12, 13)$ using a 4 X 1 (3)
- multiplexer
- 10 Differentiate combinational and sequential circuits. (3)

- 11 Draw the schematic diagram of a 3-bit parallel adder. What is the drawback of this circuit? (3)

PART D

Answer any two full questions, each carries 9 marks.

- 12 Explain how clocked sequential circuits can be designed with state equations, using an example (9)
- 13 a) Design and implement full subtractor by using only NAND gates. (5)
b) Design a 2-bit magnitude comparator. (4)
- 14 a) Explain clocked sequential circuits with an example. (4)
b) Draw and explain the logic circuit of 4-bit full adder with look ahead carry. (5)

PART E

Answer any four full questions, each carries 10 marks.

- 15 Design a Modulo 9 Synchronous counter using T FFs (10)
- 16 With neat timing diagram and sequence table explain the working of 4bit Johnson Counter using JK Flip flops. (10)
- 17 Using the circuit diagrams explain types of shift registers (10)
- 18 a) Give any 2 applications of ROM (3)
b) Explain static RAM and Dynamic RAM (4)
c) Write a note on error detection and correction. (3)
- 19 Implement the following Boolean functions using a $3 \times 4 \times 2$ PLA (10)
 $F_1 (A, B, C) = (3, 5, 6, 7)$ and
 $F_2 (A, B, C) = (0, 2, 4, 7)$.
- 20 Write an HDL code for a half adder (10)
