

**Course Code: EC201**

**Course Name: NETWORK THEORY**

Max. Marks: 100


Duration: 3 Hours

**PART A**


*Answer any two full questions, each carries 15 marks.*

Marks

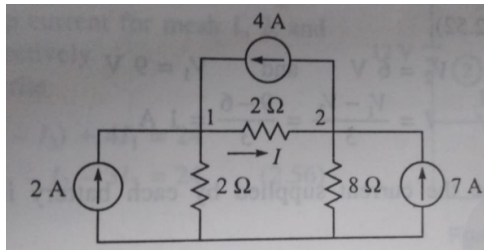
- 1 a) Using nodal analysis, find  $I$  in the circuit shown below (7)



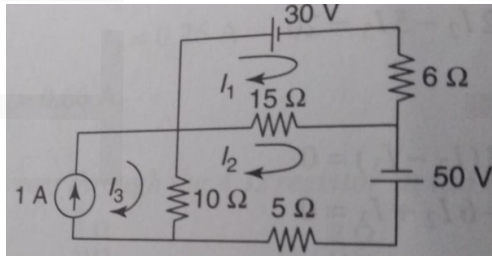
- b) Determine the mesh currents  $I_1, I_2$  and  $I_3$  in the circuit given (8)



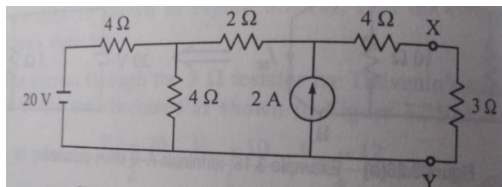
- 2 a) Determine the current through  $3\Omega$  for the circuit shown using Norton's theorem (8)



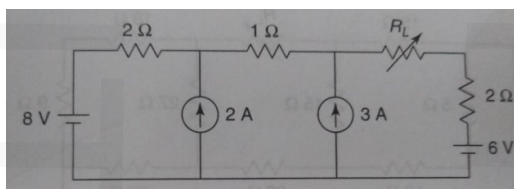
- b) For the network shown, find the value of the resistance  $R_L$  for maximum power transfer and calculate the maximum power. (7)



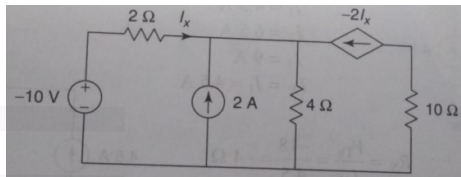- 3 a) Determine current through  $2\Omega$  resistor in the network shown in figure (8)



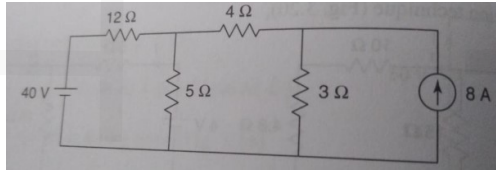
- b) Find current flowing through  $4\Omega$  resistor (7)



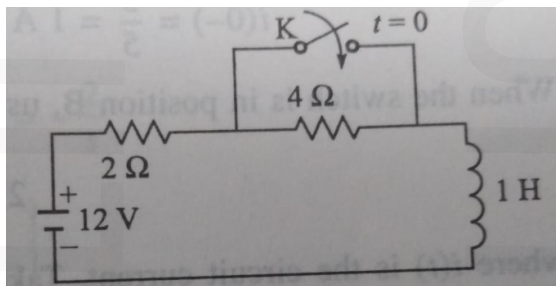
**PART B**

*Answer any two full questions, each carries 15 marks.*


- 4 a) A dc voltage is given to the circuit keeping the switch open so that steady state is reached. Determine the complete response for the circuit after closing the switch. (8)



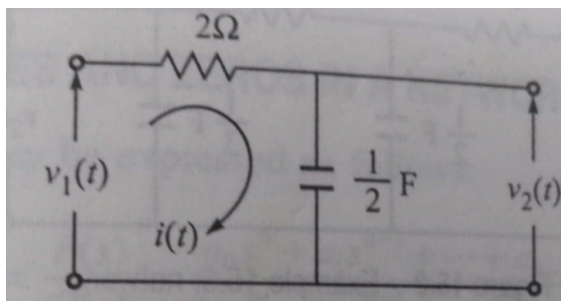
- b) Calculate the voltage transfer ratio  $V_1(s)/V_2(s)$  for the network shown below (7)



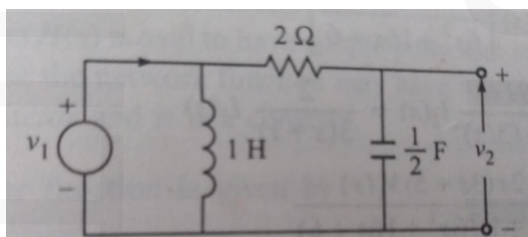
- 5 a) Determine the current transfer ratio  $\alpha_{12}(s)$  and transfer impedance  $Z_{21}(s)$  (8)



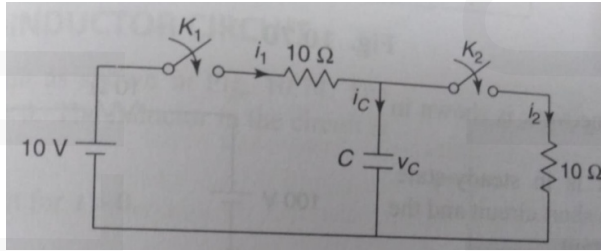- b) In the circuit shown, switch  $K_1$  has been closed for a long time prior to  $t=0$ . At  $t=0$ , the switch  $K_2$  is also closed. Find  $v_c(0^+)$  and  $i_c(0^+)$  (7)



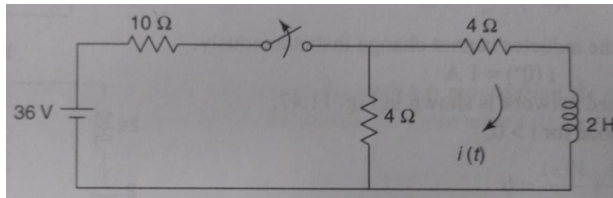- 6 a) The circuit has acquired steady state with switch closed for  $t < 0$ . At  $t=0$ , the switch is opened. Find  $i(t)$  for  $t > 0$  (8)



- b) Show the pole zero plot for the given network function  $V(s)$  and obtain  $v(t)$  (7)

$$V(s) = \frac{10s}{(s+3)(s+2)}$$


**PART C**

*Answer any two full questions, each carries 20 marks.*


- 7 a) The Z parameters of a circuit is given below. Obtain its transmission parameters (10)

$$\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$$

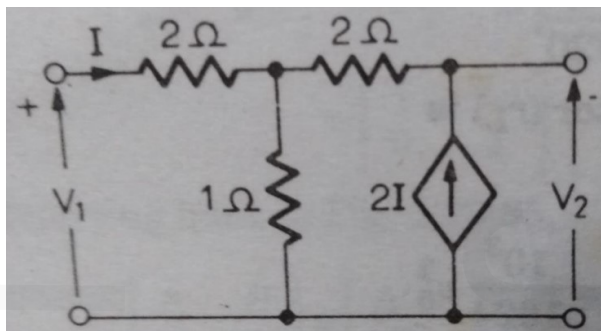
- b) Obtain open circuit parameters for the network shown (10)



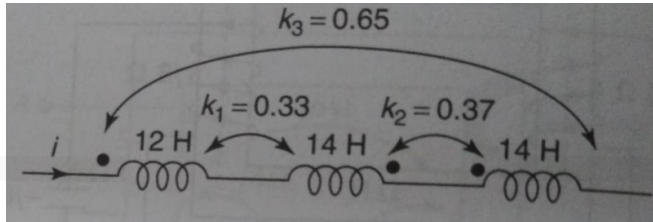- 8 a) Derive the expression for half power frequencies in series RLC resonant circuits (10)  
 b) Find the equivalent inductance of the network shown (4)



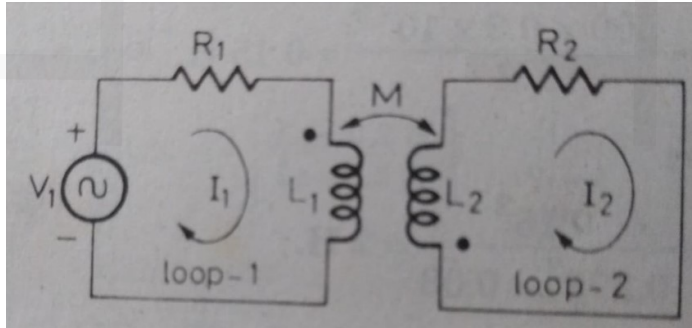- c) Write the mesh equations for the transformer circuit shown (6)



- 9 a) Currents entering port1 and port2 of a two port network are given by the following equations (10)

$$I_1 = 0.5V_1 - 0.2V_2$$

$$I_2 = -0.2V_1 + V_2$$

Find Z and ABCD parameters

- b) A non inductive resistor of  $12\Omega$ , an inductor of  $0.2\text{H}$  and a capacitor of  $9\mu\text{F}$  are connected in series. Calculate (i) the resonance frequency (ii) current at resonant frequency (iii) the voltage across each component when a voltage of  $35\text{V}$  at resonant frequency is applied to the whole circuit. (10)

\*\*\*\*