

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree (S,FE) Examination January 2022 (2015 Scheme)

Course Code: EC205**Course Name: ELECTRONIC CIRCUITS (EC,AE)**


Max. Marks: 100

Duration: 3 Hours

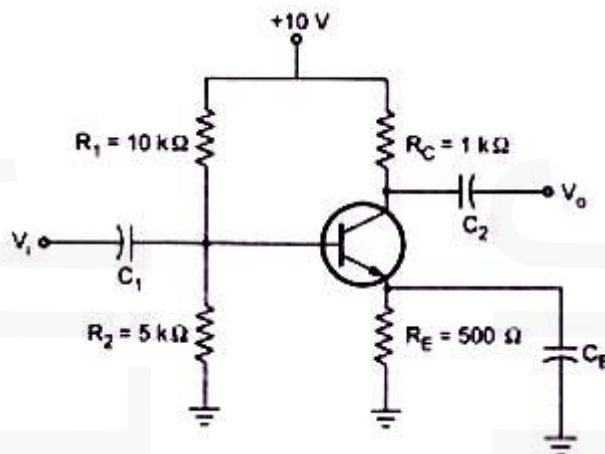
PART A*Answer any two full questions, each carries 15 marks.*

Marks

- 1 a) For the given circuit $\beta=100$ for silicon transistor. Calculate the operating points. (7)
Assume data that are not given.



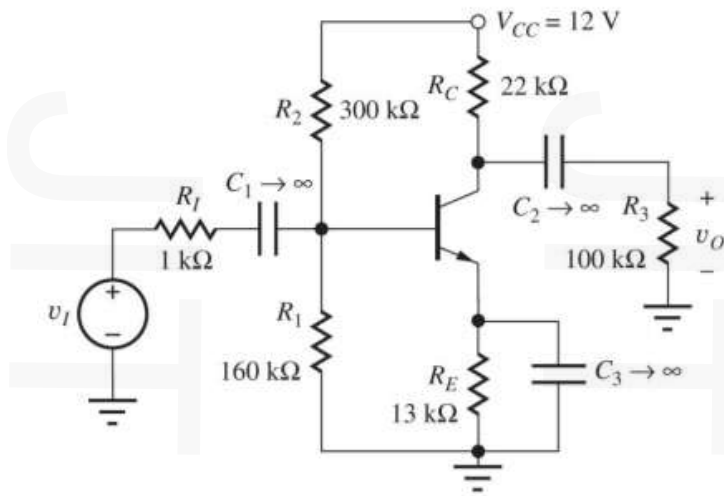- b) With a neat circuit diagram, design a RC integrator circuit for an input frequency of $f = 1$ kHz. (4)
- c) Explain the concept of ac and dc load line. (4)
- 2 a) Derive the condition for a high pass RC circuit to behave as a differentiator. (5)
- b) What is bias stability? Derive the stability factor for leakage current of a collector to base bias transistor circuit. (7)
- c) Obtain the transfer function for a low pass filter. (3)
- 3 a) Draw the small signal hybrid II model of the given circuit. Assume data not given. (8)



- b) Derive the expression for voltage gain of a two-stage cascade amplifier. (7)

PART B

Answer any two full questions, each carries 15 marks.

- 4 a) What is Miller effect? (3)
- b) From the high frequency equivalent circuit, derive the expression for beta cut off frequency of a bipolar transistor. Draw the frequency response for short circuit current gain. (9)
- c) What are the conditions for sustained oscillation? (3)
- 5 a) Find mid-frequency voltage gain and output impedance of a CE amplifier without bypass capacitor using hybrid Π model. (7)
- b) Draw the circuit diagram of cascode amplifier. (4)
- c) Explain the working of an LC tank circuit. (4)
- 6 a) Draw the circuit diagram of a Hartley oscillator. In Hartley Oscillator $L_1=0.3\text{mH}$, $L_2=0,3\text{mH}$ and $C=0.003\mu\text{F}$. Calculate the frequency of oscillation. (4)
- b) What are different feedback topologies? Explain how the current series feedback effect the input and output impedances. (7)
- c) Differentiate between synchronous and stagger tuning. (4)

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) A class-B push pull amplifier working with $V_{cc}=25\text{V}$ provides a 22V peak signal to a 8Ω load. Calculate the amplifier efficiency and power dissipated per transistor. (5)

- b) With a neat circuit diagram, explain the working of a series voltage regulator with error amplifier. (7)
- c) Draw the circuit diagram of a bistable multivibrator and explain its working with relevant waveforms. (8)
- 8 a) With neat circuit diagrams and waveforms, explain the working of a transistor bootstrap sweep generator circuit. What are its applications? (10)
- b) Draw the circuit diagram of a class AB push pull amplifier and explain its working. (6)
- c) What is cross over distortion in amplifiers? How it is solved. (4)
- 9 a) Draw the circuit diagram of a transistor shunt voltage regulator and explain its working. (8)
- b) Differentiate between line and load regulations. (6)
- c) Draw and explain the working of a Schmitt trigger. (6)
