

B3B053

Reg. No. _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
THIRD SEMESTER B.TECH DEGREE EXAMINATION, JULY 2017

Course Code: **EC 201**

Course Name: **NETWORK THEORY (AE,EC)**


Max. Marks: 100

Duration: 3 Hours


PART A

Question No. 1 is compulsory.

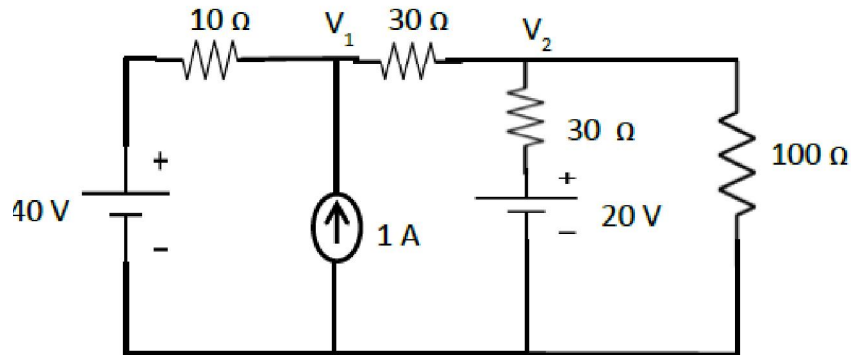
1. a) State Kirchhoff's current law. (2)
- b) Find the current in 100Ω resistor using nodal analysis. (5)



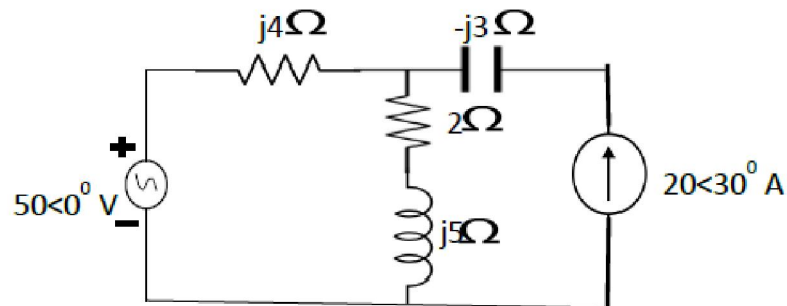
- c) State super position theorem. (2)
- d) Using super position theorem find the voltage across $(2+j5)\Omega$ impedance for the network shown. (6)



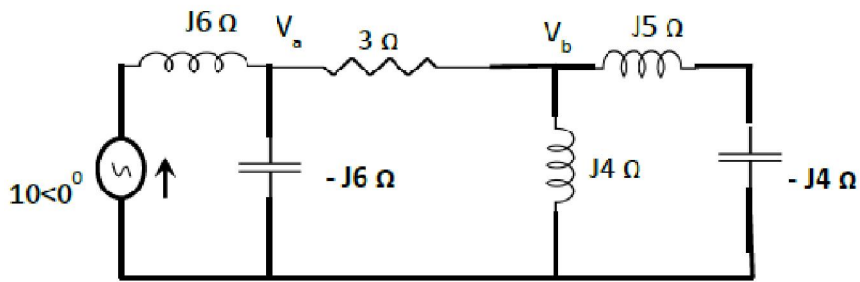2. a) Differentiate between (i) tree and co tree (ii) links and twigs. (2)
- b) Determine V_a and V_b , from the given circuit. (7)




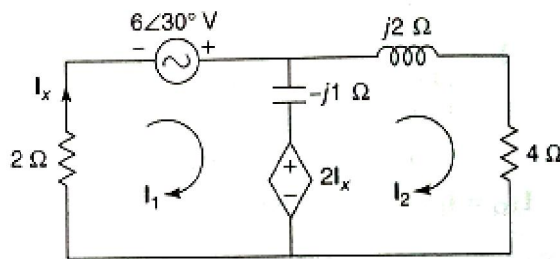c) In the network find the voltage across the 4Ω resistor. (6)



OR

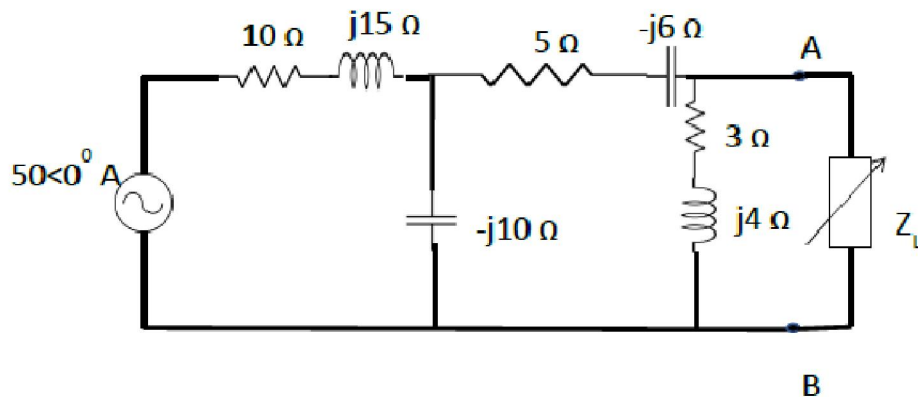- 3. a) State and Prove maximum Power transfer theorem. (3)
- b) Determine the maximum power delivered to the load. (4)




- c) State and prove time integration theorem. (4)
- d) Find Lapalce transform of (i)(1-e^{-t})/t (ii)(t+1)²e^t (4)

PART B


Question No. 4 is compulsory.

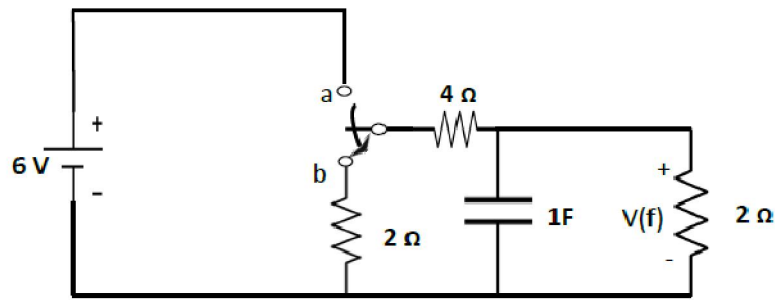- 4. a) In the network shown the switch is moved from a to b (steady state was achieved in position a). Find v(f). (6)



b) List any 5 properties of transfer functions. (5)

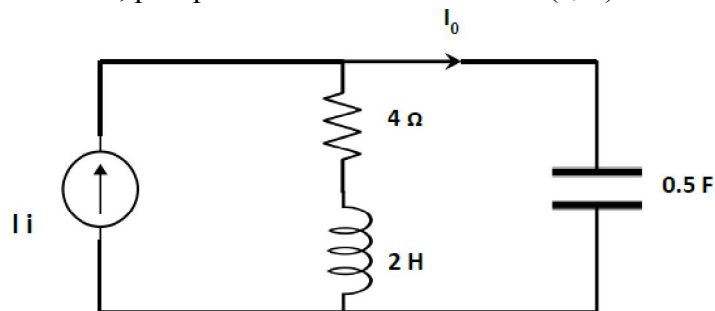
c) In the network shown, plot poles and zeros function of (I_o/I_i) (4)



5. a) Find inverse Laplace transform of $(2s+1)/(s^2+2)(s+1)$. (4)

b) Solve $y'' - y = t, y(0) = 1, y'(0) = 0$ (5)

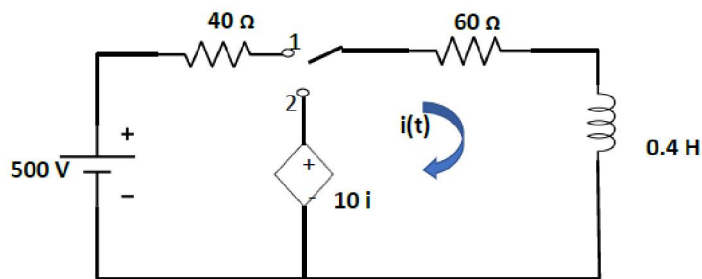
c) For the network shown, find the current $i(t)$ when the switch is changed from position 1 to 2 at $t=0$



(6)

OR

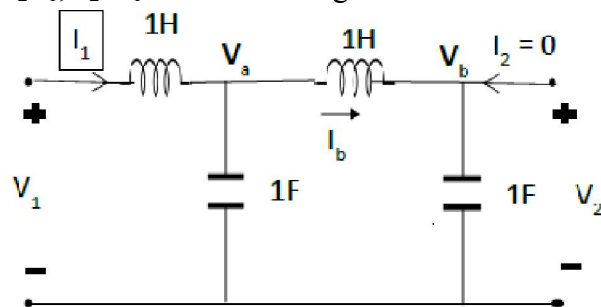6. a) Obtain the $Z_{11}, V_2/I_1, V_2/V_1$ of the following network. (10)




- b) Plot the magnitude and phase response for the transfer function, V_2/V_1 of an RC two port network (Integrator) (5)


PART C

Question No. 7 is compulsory.

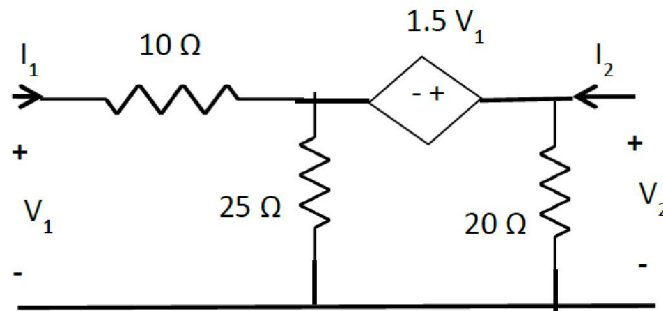
7. a) Find the transmission parameters for the two port network shown. (8)



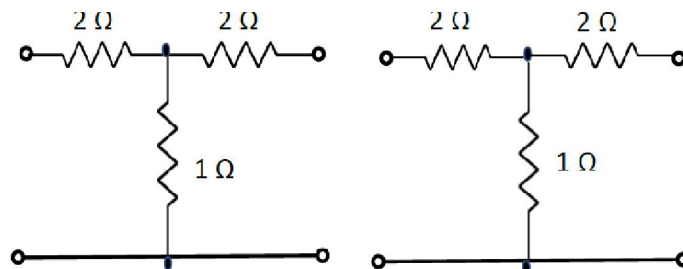- b) Two identical sections of a network shown in the figure are connected in series. obtain the Z parameters of the combination and verify by direct calculation (8)



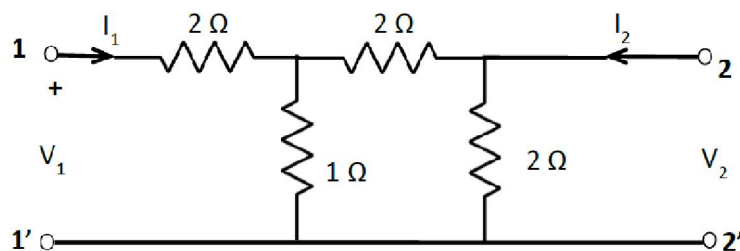- c) Define resonance. Find the condition for resonance in a series RLC circuit (4)
 8. a) For the network shown, derive the open circuit admittance parameters and draw its equivalent circuit (10)



- b) Express Z parameters in terms of hybrid and inverse hybrid parameters. (10)

OR

9. a) A series RLC circuit has $R=25\Omega$, $L=0.41H$, $C=0.01\mu F$. calculate the resonant frequency. If 1V source of the same frequency as the resonant frequency is

applied to this circuit, calculate the frequencies at which the voltage across L and C is maximum. Calculate the voltages. (8)

b) Consider a single tuned circuit. Determine the resonant frequency, the output voltage at resonance and the maximum output voltage. Assume $R_s \gg \omega_r L_1$ and $K=0.9$ (12)

