

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FOURTH SEMESTER B.TECH DEGREE EXAMINATION, APRIL 2018

Course Code: EC204

Course Name: ANALOG INTEGRATED CIRCUITS (AE, EC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

Marks

- | | | |
|---|---|-----|
| 1 | a) Derive CMRR, input resistance and output resistance of a dual input balanced output differential amplifier configuration. (8) | (8) |
| | b) Define the following: (3) | (3) |
| | i) Input bias current ii) Input offset current iii) Input offset voltage | |
| | c) Implement the equation using two op-amps (4) | (4) |
| | $V_0 = -5V_1 + 2V_2 - 10V_3$ | |
| 2 | a) Derive the following characteristics of voltage shunt amplifier: (8) | (8) |
| | i) Closed loop voltage gain ii) Input resistance | |
| | iii) Output resistance iv) Bandwidth | |
| | b) What is slew rate? Derive an equation for it. (4) | (4) |
| | c) A differential amplifier has a common mode gain of 0.05 and difference mode gain of 1000. Calculate the output voltage for two signals $V_1 = 1\text{mV}$ and $V_2 = 0.9\text{mV}$ (3) | (3) |
| 3 | a) Explain the variation of differential gain of a differential amplifier with frequency of operation with relevant expressions. (5) | (5) |
| | b) Draw the circuit diagram of a differential instrumentation amplifier with a transducer bridge and show that the output voltage is proportional to the change in resistance. (7) | (7) |
| | c) How a constant current bias circuit can be used to improve the CMRR of a differential amplifier? (3) | (3) |

PART B

Answer any two full questions, each carries 15 marks.

- | | | |
|---|--|-----|
| 4 | a) Draw the circuit of a temperature compensated logarithmic amplifier and show that it provides temperature independent logarithmic output. (8) | (8) |
| | b) Explain the working of a triangular waveform generator with a neat circuit diagram. Also derive an expression for frequency of oscillation. (7) | (7) |
| 5 | a) Draw the circuit of a Wien Bridge oscillator using op-amp and derive an equation for frequency of oscillation. (7) | (7) |
| | b) With a neat circuit diagram explain the working of astable multivibrator using op-amp. Also derive an expression for time period. (8) | (8) |
| 6 | a) Draw the circuit of second order low pass filter and derive its transfer function. (8) | (8) |
| | b) Draw the circuit of a precision full-wave rectifier and explain its working. (7) | (7) |

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Explain how a monostable multivibrator can be implemented with 555 IC with relevant waveforms and functional diagram. Derive an expression for pulse width. (10)
- b) With a neat circuit diagram, explain the operation of a 3-bit flash converter. (10)
- 8 a) With a neat block diagram explain the working of PLL. Explain any two applications of PLL. (10)
- b) Explain the working of dual-slope ADC with a neat circuit diagram. (10)
- 9 a) Explain how short circuit, fold back protection and current boosting are done using IC723 voltage regulator. (10)
- b) With a neat circuit diagram explain the working of a weighted resistor D/A converter (10)
