

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FIFTH SEMESTER B.TECH DEGREE EXAMINATION(R&S), DECEMBER 2019

Course Code: EE305

Course Name: POWER ELECTRONICS

Max. Marks: 100

Duration: 3 Hours

Graph sheet may be supplied on demand

PART A

Answer all questions, each carries 5 marks.

Marks

- | | | |
|---|--|-----|
| 1 | Sketch the static VI characteristics of SCR and define latching current and holding current. | (5) |
| 2 | Describe briefly the RC triggering circuit for SCR with a neat circuit diagram. With the help of a graph explain how firing angle control up to 180 degrees is obtained. | (5) |
| 3 | Explain the operation of three-phase dual converter with circulating current.. | (5) |
| 4 | Sketch the diagram and output voltage waveform of a single phase half bridge Voltage Source Inverter with R load and describe the working. | (5) |
| 5 | Define modulation index and Frequency modulation ratio. | (5) |
| 6 | What are the control strategies for the regulation of output voltage in AC Voltage Controllers? | (5) |
| 7 | Explain the different methods by which control of output voltage is obtained in Choppers. | (5) |
| 8 | Derive the expression for the voltage gain in a Boost regulator. | (5) |

PART B

Answer any two full questions, each carries 10 marks.

- | | | |
|----|---|-----|
| 9 | a) Compare the characteristic features of MOSFET AND IGBT | (4) |
| | b) Give the structure and operation of TRIAC. | (6) |
| 10 | a) Describe a single phase half controlled converter with RL load along with necessary circuit diagram and waveforms. | (4) |
| | b) With neat circuit diagram explain the operation of a Single Phase Half Wave Rectifier with R, load. Sketch the shape of output voltage waveform. | (6) |
| 11 | a) Explain how di/dt and dv/dt protection is accomplished in SCR. | (4) |

- b) A fully controlled full wave converter has a source of 240 V rms, 50 Hz and $10\ \Omega$, 50mH, 50V Emf opposing series load. The delay angle is 45° . Determine (6)
- a) Average output voltage and current.
 - b) Rms load voltage and Rms voltage across the RL part of the load.
 - c) The power absorbed by the 50V load back emf.

PART C

Answer any twofull questions, each carries 10 marks.

- 12 Sketch the circuit diagram and explain the working of a 3 phase full wave controlled rectifier with RLE load. Draw the output voltage waveforms corresponding to $\alpha = 60^\circ$, $\alpha = 90^\circ$ and $\alpha = 150^\circ$ (10)
- 13 Draw the circuit and explain the 180° operation of a 3 phase bridge inverter with R load. Draw the phase voltage and line voltage waveforms. (10)
- 14 a) With necessary waveforms explain the working and four quadrant operation of a single phase circulating current type Dual converter. (5)
- b) Differentiate a Current source inverter from a Voltage source Inverter. (5)

PART D

Answer any twofull questions, each carries 10 marks.

- 15 Explain with relevant waveforms a Single phase AC voltage controller with RL load. (10)
- 16 How four-quadrant operation is achieved in a Type E Chopper? Explain with neat circuit diagram. (10)
- 17 a) What is meant by Pulse Width Modulation? Describe the various PWM techniques used in Voltage control of Inverters. (5)
- b) Explain Sequence control with R load. (5)
