



Reg. No. :

Name :


Third Semester B.Tech. Degree Examination, November 2010
(2008 Scheme)
P 10.104/08.305 : DIGITAL SYSTEM DESIGN (R1P)

Time : 3 Hours

Max. Marks : 100

PART – A

(Answer all questions)

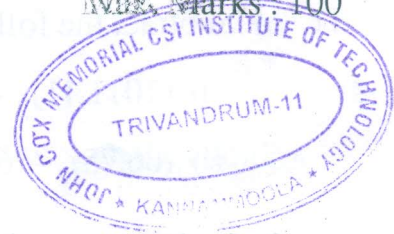

1. Subtract the following decimal numbers using (r-1)'s complement method of addition.
 - a) $1075.56 - 876.14$
 - b) $34.375 - 1210.8$
2. Obtain the weighted binary code for the base-12 digits using weights of 5421.
3. Convert the following numbers to decimal.
 - a) $(ACF.0E)_{16}$
 - b) $(1354.012)_6$
 - c) $(1231.120)_4$
 - d) $(8753.8130)_9$
4. List the six postulates of Boolean algebra.
5. Simplify the following expression and realize it using NAND gates
 $f = xy + x'z + yz$.
6. Obtain the simplified boolean function for the two outputs of a full subtractor.
7. Simplify the following function as product of sums form using k-map.
 $f(a, b, c, d) = \Sigma (1, 3, 5, 6, 7, 15)$
8. Differentiate between synchronous and asynchronous counters.
9. Explain the working of a JK flip flop.
10. Write notes on shift registers.



PART – B

(Answer **any one** full question from **each** Module)**Module – I**

11. a) Subtract the following numbers using complement method of addition.

i) $(1011.11)_2 - (101.110)_2$

ii) $(ABCD.189)_{16} - (1798B.AC)_{16}$

iii) $(66.75)_8 - (6754.431)_8$

iv) $(9813.65)_{BCD} - (758.458)_{BCD}$ **12**

b) Write notes on the following codes :

i) Excess - 3 code

ii) Gray code

iii) ASCII

iv) EBCDIC. **8**

OR

12. a) Perform the following operation without converting the numbers to decimal

i) $(1212.10)_3 + (10012)_3$

ii) $(5487)_9 + (81)_9$

iii) $(453.06)_7 + (1026.1)_7$

iv) $(145)_6 + (15.3)_6$ **8**

b) If r is the base of a number system, explain how do you perform subtraction using r 's complement addition. Give two examples. **12****Module – II**13. a) Design an excess-3 to BCD code converter. **8**

b) Express the following function in sum of min. terms and product of max. terms and also simplify the same using k-map.

i) $f(A, B, C, D) = (A + B' + C) \cdot (A + B') \cdot (A + C + D') \cdot (A' + B + C + D') \cdot (B + C' + D')$

ii) $f(x, y, z) = (xy + z)(y + xz)$ **12**

OR



14. a) Implement the following boolean function.

$$f = xy + x'y' + y'z'$$

Using

i) AND, OR and NOT gates

ii) Only NOR gates

iii) Only NAND gates.

8

b) Show how a Full Adder can be converted to a Full Subtractor with the addition of one inverter circuit.

12

Module – III

15. a) Design a 4-bit Binary Ripple Counter.

15

b) Write notes on Hardware Description Language.

5

OR

16. a) Explain the working of both D and T flipflops.

12

b) Give the circuit diagram for a 4-bit synchronous Binary counter.

8