



Reg. No. : .....

Name : .....

**Third Semester B.Tech. Degree Examination, September 2014**  
**(2008 Scheme)**  
**(Special Supplementary)**  
**08.305 : DIGITAL SYSTEM DESIGN (RF)**

Time : 3 Hours

Max. Marks : 100

PART - A



Answer **all** questions :

1. Represent the decimal number 1875 in
  - a) BCD code
  - b) Excess-3 code
  - c) As hexadecimal
  - d) As octal.
2. Determine the radix 'r' :
  - i)  $(365)_r = (194)_{10}$
  - ii)  $(BEE)_r = (2699)_{10}$ .
3. What are self complementing codes ? Give an example.
4. Show that :
  - a)  $a + a'b = a + b$
  - b)  $x'y'z + x'yz + xy' = x'z + xy'$
5. A circuit receives a 4-bit Excess-3 code. Design a minimal circuit to detect the decimal numbers 0, 1, 4, 6, 7 and 8.
6. Implement the following function  
 $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$  with exclusive-OR and AND gates.
7. Differentiate between a decoder and a demultiplexer.



8. What do you mean by race condition in a flip-flop ? How can it be eliminated ?
9. What is the difference between serial and parallel transfer ? What type of register is used in each case ?
10. Explain the principle of a shift register. (10×4=40 Marks)

### PART – B

Answer **any one** from **each** Module.

#### Module – I

11. a) Convert the following as indicated :
  - i)  $(2021.102)_3$  to base 9
  - ii)  $(ADE.B)_{16}$  to base 4
  - iii)  $(134.12)_5$  to base 7
  - iv)  $(384.74)_{10}$  to binary
  - v)  $(756.603)_8$  to hexadecimal. 15
- b) Differentiate between a weighted and an unweighted code. Give examples for each. 5

OR

12. a) Perform the arithmetic operations :
  - a)  $10111.101 + 110111.01$
  - b)  $10001.01 - 1111.11$
  - c)  $1101.11 \times 101.1$
  - d)  $1011110 \div 1001$  12
- b) Explain briefly on error detection and error correction codes. 8

#### Module – II

13. a) Express the following functions in a sum of minterms and a product of maxterms :
  - i)  $F(A, B, C, D) = D(A' + B) + B'D$
  - ii)  $F(w, x, y, z) = y'z + wxy' + wxz' + w'x'z$ . 8



b) Reduce the function

$f(A, B, C, D) = \sum m(2, 3, 6, 7, 9, 12, 13, 14) + \sum d(4, 5)$  using tabulation method and realize using NAND gates.

12

OR

14. a) Give the simplified expression for the following function where d represents don't care condition. Represent the simplified function using logic gates.

$f(A, B, C, D) = \sum m(0, 8, 11, 12, 15) + \sum d(1, 2, 4, 7, 10, 14)$

10

b) Design and implement a 4-bit gray code to binary converter.

10

### Module – III

15. Explain the working of a T flip-flop. Design a counter using T flip-flops that has a repeated binary sequence of states 0, 1, 3, 7, 6, 4.

20

OR

16. a) With a neat diagram explain the working of master slave flip flop.

10

b) Construct a 4-bit ring counter. Draw the timing diagram and explain its working.

10

