



(Pages : 2)

A – 6595

Reg. No. : .....

Name : .....

**Third Semester B.Tech. Degree Examination, October 2016  
(2013 Scheme)**

**13.305 : DIGITAL SYSTEM DESIGN (FR)**

Time : 3 Hours

Max. Marks : 100

John Cox Memorial CSI Institute of Technology  
Kannamcola, Thiruvananthapuram  
695011

**PART – A**

Answer **all** questions. **Each** question carries **2** marks.

1. Express the Boolean function  $F = A' + B'C$  as a sum of minterms.
2. Design a Half Adder Circuit.
3. Simplify the following Boolean expression using K-map.  
 $F = x'yz + x'yz' + xy'z' + xy'z$ .
4. Draw the logic diagram of D-Flip-flop with NAND gates. Briefly discuss the operation of the circuit.
5. Implement  $F(A, B, C) = \sum(1, 3, 5, 7)$  with a Multiplexer.
6. What is meant by loading a register ? Explain.
7. Differentiate between synchronous and asynchronous counters.
8. Draw the timing diagram for BCD Counter.
9. How the divide overflow problem can be avoided ?
10. Differentiate between restoring and non-restoring division.

P.T.O.



## PART - B

Answer **one full** question from **each** Module. **Each** question carries **20** marks.

**Module - I**

11. a) The following Boolean expression  $BE + B'DE'$  is a simplified version of the expression  $A'BE + BCDE + BC'D'E + A'B'DE' + B'C'DE'$ . Are there any don't care conditions? If exists, what are they?
- b) Obtain the simplified form of the given expression as a Sum of Products  
 $F(A,B,C,D) = A'B'C'D' + AC'D' + B'CD' + A'BCD + BC'D$ .
12. a) Simplify the following Boolean expression by using Tabulation Method.  
 $F = \sum(0, 1, 2, 8, 10, 11, 14, 15)$
- b) Implement a full subtractor with 2 half subtractors and an OR Gate.

**Module - II**

13. a) Design a combinational circuit that converts a Decimal digit from 8, 4, -2, -1 code to BCD.
- b) Design a Carry Look Ahead Adder Circuit.
14. a) Discuss the working of a clocked JK Flip-flop.
- b) Is it possible for a decoder to function as a Demultiplexer? If yes, explain how?

**Module - III**

15. a) Discuss the working of BCD Ripple Counter. 15
- b) What is meant by memory decoding? Explain. 5
16. a) Design a BCD to Gray code converter.
- b) Design a  $2 \times 4$  Decoder in HDL.

**Module - IV**

17. a) Explain Booth's Multiplication Algorithm with an example.
- b) Give an algorithm for the multiplication of two BCD numbers.
18. a) Discuss an algorithm for the addition of 2 Floating point numbers.
- b) Discuss the working of an Array Multiplier.