



(Pages : 2)

8721

Reg. No. : .....

Name : .....

**Third Semester B.Tech. Degree Examination, December 2015  
(2008 Scheme)**

**Branch : Electronics & Communication Engineering  
08.306 : DIGITAL ELECTRONICS (T)**

Time : 3 Hours

Max. Marks : 100

**PART - A**

Answer **all** questions. **Four** marks **each**.

1. Using De Morgan's Theorems, find the equivalent to  $F = ab + ac$ .
2. Find the minimal POS using k-map  $P = \pi (0, 2, 5, 7, 8, 10, 13, 15)$ .
3. Write VHDL programme for a half adder.
4. What are the input and output logic levels of CMOS ?
5. What are the advantages of edge triggered flip flops over level triggered one ?
6. Distinguish between positive and negative logic.
7. Design a monostable multivibrator using 74121 to obtain a pulse of width 100 ms.  
Draw the circuit diagram.
8. Draw a asynchronous machine model and explain.
9. What are races and cycles that exist in asynchronous machines ?
10. What are the guidelines for making a state assignment ?



P.T.O.



## PART – B

Answer **any 2** questions from **each** Module. **Each** question carries **10** marks.

## Module – 1

11. Using Quine Mc Cluskey method, simplify  
 $F = \sum(1, 3, 13, 15) + \sum d(8, 9, 10, 11, 12)$
12. Design a 2 digit BCD adder using 74LS83.
13. a) Design and implement a 3 bit look ahead carry adder.  
 b) What are the differences between static RAM and Dynamic RAM ?

## Module – 2

14. a) Explain the operation of a ECL OR/NOR gate.  
 b) What are the applications of open collector gates ?
15. Design a counter to count the sequence 3-2-5-7-6-3.
16. a) Draw the circuit of a 5-bit ring counter and explain its working.  
 b) What is race-around condition ? How it can be eliminated ?

## Module – 3

17. a) Define state variable and excitation variable with example.  
 b) Explain the steps for synchronous sequential circuits analysis.
18. Create a shared row state assignment for the following flow table.

Present State	Next State			
	00	01	10	11
a	(a)	b	(a)	b
b	c	(b)	(b)	(b)
c	(c)	d	b	d
d	(d)	(d)	a	(d)

19. a) Explain static hazards, dynamic hazards and essential hazards with examples.  
 b) Design a hazard free combinational circuit "  
 $f = \sum(0, 1, 3, 4, 5, 12, 13)$