



Reg. No. :

Name :

Third Semester B.Tech. Degree Examination, November 2013
(2008 Scheme)
08.303 : NETWORK ANALYSIS (TA)

Time : 3 Hours


Max. Marks : 100

PART - A




Answer **all** questions.

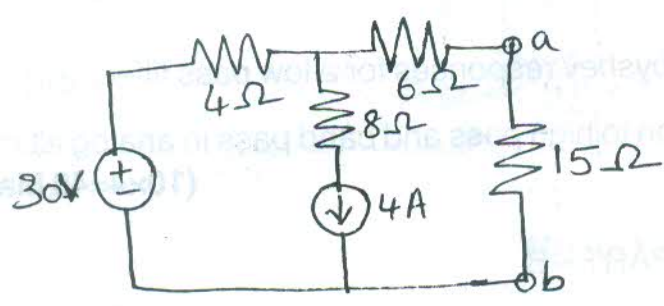1. Find the Norton's equivalent circuit across terminals ab for the circuit shown below.



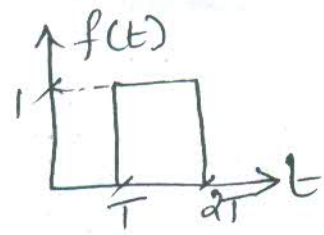
2. Obtain the expression for the given function, $f(t)$ in terms of unit step function



3. State and prove initial value theorem.



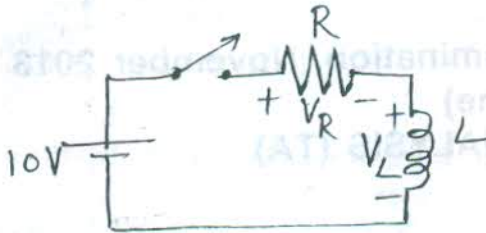4. For the series RL circuit shown below, a constant voltage is applied at $t = 0$. At what time does $V_R = V_L$.




5. Derive the expressions for Z-parameters of a two port network in terms of Y-parameters.
6. Design a symmetrical T-type attenuator with characteristic impedance, R_0 and attenuation, N .
7. What are Bode plots ? Define Gain margin and phase margin.
8. Determine the quality factor of a coil for the series circuit consisting of $R = 10\Omega$, $L = 0.1\text{H}$ and $C = 10\mu\text{F}$.
9. Compare the Butterworth and Chebyshev responses for a low pass filter.
10. Explain the frequency transformation to high pass and band pass in analog filter design. (10x4=40 Marks)

PART - B

Answer **any two** questions from **each** Module. **Each** question carries **10** marks.


Module - I

11. Using node analysis, determine i_x .

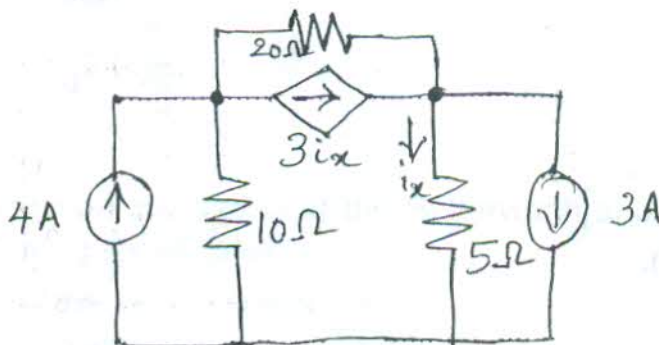




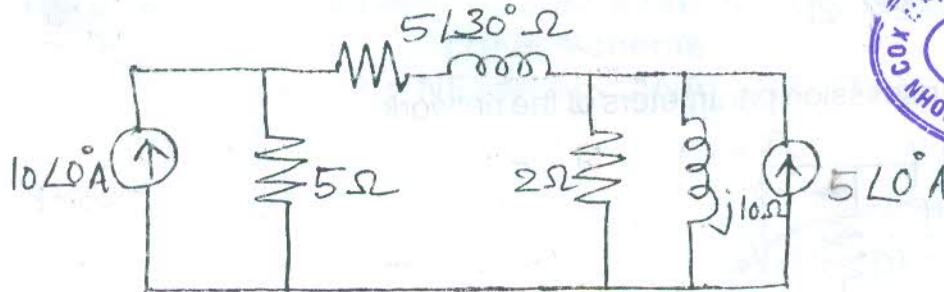12. In the circuit shown below, determine the voltage across 2Ω resistor using superposition theorem.




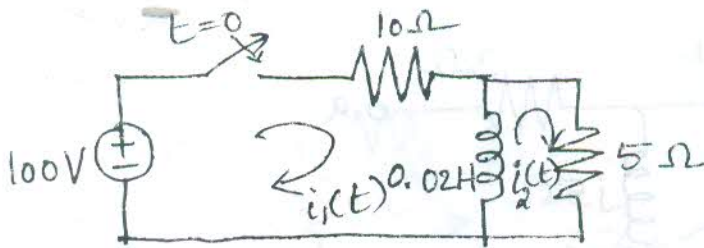13. In the circuit shown, find the current $i_1(t)$ and $i_2(t)$ which results when the switch is closed at $t = 0$.



Module - II

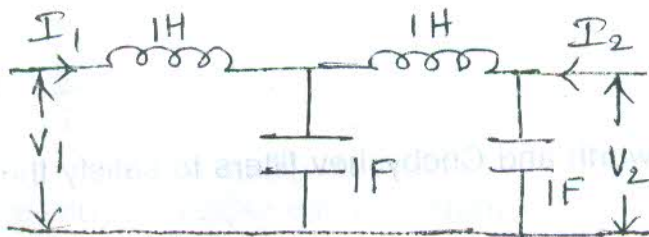14. a) What are the necessary conditions for the network function to be a driving point function? 4
- b) For the given network, find the driving point impedance, $Z_{11}(s)$ and voltage transfer ratio, $G_{12}(s)$. 6






15. Draw the pole-zero diagram and hence obtain the time domain response, $V(t)$ from the pole-zero plot for the network function


$$V(s) = \frac{5s}{(s+3)(s^2+2s+2)}$$

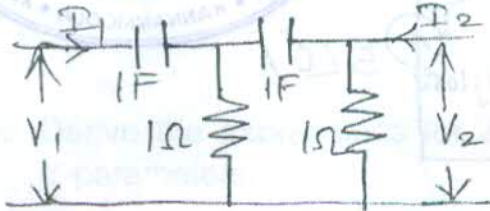16. Determine the transmission parameters of the network




Module – III

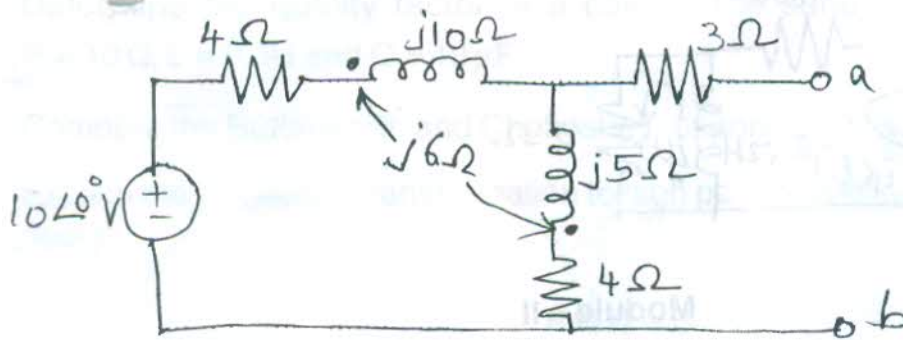17. Obtain Thevenin's equivalent circuit at terminal ab for the coupled circuit shown below



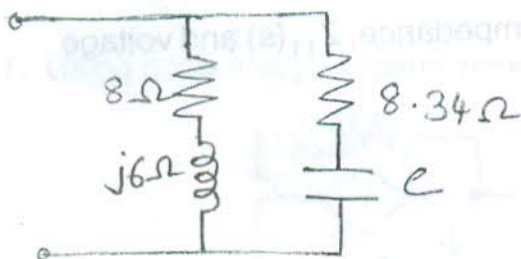18. For the circuit shown, find the value of capacitance, C so that the circuit resonates at a frequency of 5000 rad/sec.



19. Determine the orders of the Butterworth and Chebyshev filters to satisfy the following specifications.

$$\alpha_p \leq 1\text{dB}, \quad \omega \leq 150\text{Krad/sec}$$

$$\alpha_s \geq 60\text{dB}, \quad \omega \geq 200\text{Krad/sec.}$$

(6×10=60 Marks)