



Reg. No. :

Name :

**Third Semester B.Tech. Degree Examination, September 2014
(2008 Scheme)
(Special Supplementary)
08.303 : NETWORK ANALYSIS (TA)**


Time : 3 Hours

Max. Marks : 100


PART - A

Answer **all** questions, **each** question carries **four** marks.

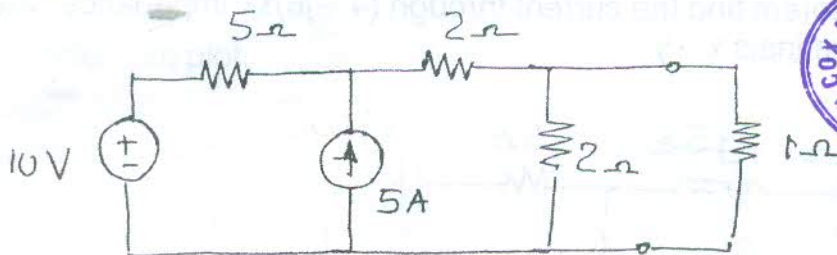1. State and prove maximum power transfer theorem in ac circuits.
2. Find the current through $1\ \Omega$ resistor using Norton's theorem.



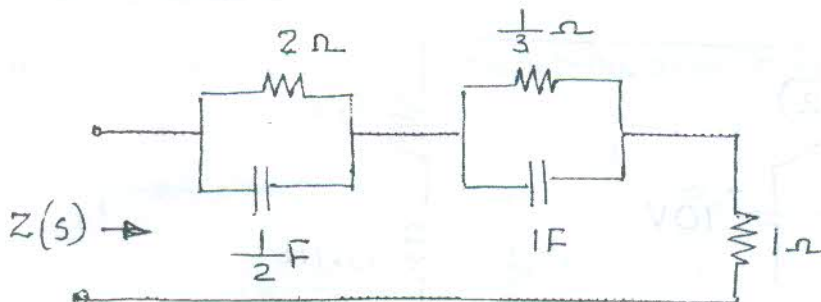3. State and prove initial and final value theorems.
4. Plot the following function
 - a) $u(t - 6) + u(t - 4)$
 - b) $5u(t + 4)$
 - c) $\delta(t + 5)$
 - d) $4r(t - 3)$
5. Find the driving point impedance $z(s)$ of the network shown






6. What is gain margin and phase margin ?
7. A network function is given by $P(s) = \frac{2s}{(s+2)(s^2+2s+2)}$ obtain the pole-zero diagram.
8. Explain the terms resonance, bandwidth and Q-factor.
9. What is characteristic impedance and propagation constant ?
10. What is the significance of Bessel Thomson response.

PART - B


Answer **any two** questions from **each** Module. **Each** question carries **10** marks.

Module - I

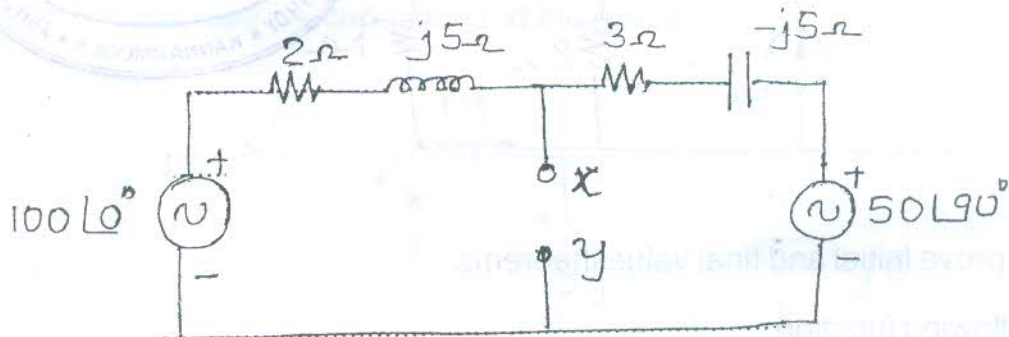11. Using Thevenin's theorem find the current through $(4 + j6)\Omega$ impedance when connected across terminals x - y.




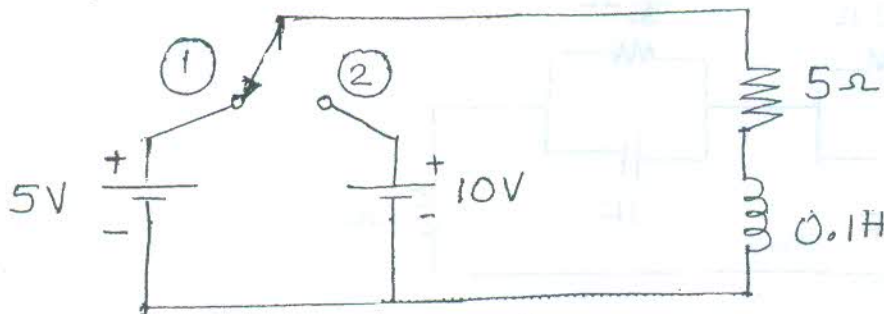12. Obtain the expression for the current $i(t)$ when the switch is moved from position 1) to position 2) at $t = 0$.






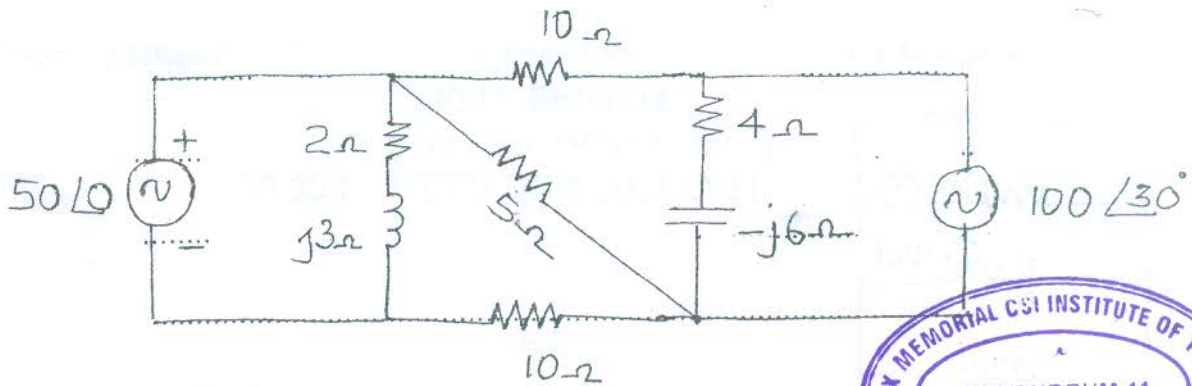13. Find by the principle of super position the current through 5Ω resistor.



Module - II

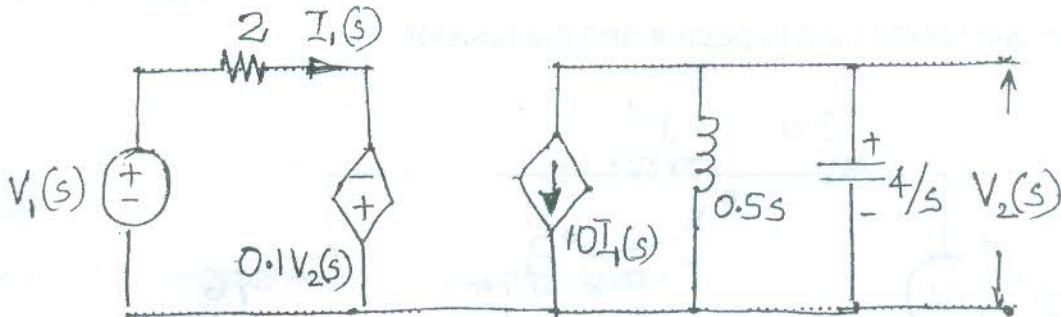
14. Find the driving point admittance function $\frac{I_1(s)}{V_1(s)}$ of the given network and its pole-zero plot.



15. Draw the Bode plot for $G(s) = \frac{20}{s(s+10)(s+2)}$. From the Bode plot determine

- a) phase cross-over frequency
- b) gain cross over frequency
- c) gain margin
- d) phase margin.

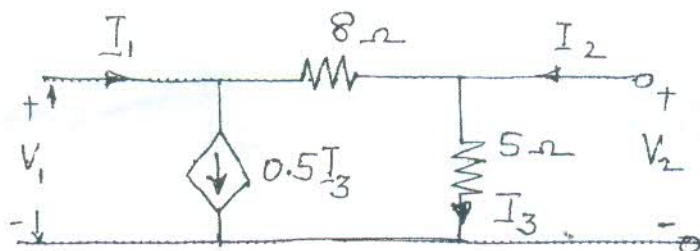16. Obtain the z parameters of the network shown in figure






Module – III

17. Obtain the resonant frequency of the circuit

$$R_c = 10\Omega \quad L_c = 0.1H$$

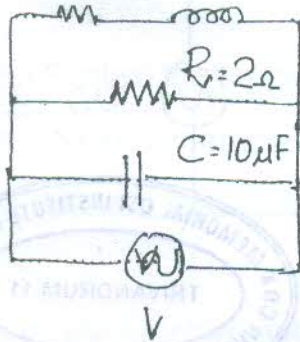

18. Find the Butterworth transfer function that meets the following specifications

$$\text{DC gain} = 1 \quad f_p = 10 \text{ KHz} \quad A_{\text{max}} = 1 \text{ dB} \quad f_s = 15 \text{ KHz} \quad A_{\text{min}} = 25 \text{ dB}$$

19. Find the drop across the capacitor and the resistor.

