



(Pages : 2)

A – 4186

Reg. No. :

Name :

**Fourth Semester B.Tech. Degree Examination, June 2016
(2013 Scheme)**

13.402 : DIGITAL ELECTRONICS AND LOGIC DESIGN (E)

Time : 3 Hours

Max. Marks : 100

PART – A

Answer **all** questions :

(10×2=20 Marks)

1. Realize an XOR gate using NOR gates.
2. i) Convert $(378.93)_{10}$ to octal.
ii) Convert $(756.603)_8$ to hexa decimal.
3. What is fan in and fan out ?
4. Realize a circuit which can generate parity bit for the given four bit data.
5. Compare a multiplexer and demultiplexer.
6. How will you convert RS flip-flop into JK flip-flop ?
7. What is the difference between level triggering and edge triggering ?
8. What is race around problem ?
9. Explain EPROM.
10. What are the basic classifications of RAM ?



PART – B

Answer **any one** question from **each** Module :

Module – I

11. a) Reduce the expression using K map and implement the function using NAND gate
 $\Sigma m = (0, 1, 4, 5, 6, 7, 9, 11, 15) + d (10, 14)$. 10
- b) What are universal gates ? Why are they called universal ? 5
- c) What is gray code ? Find the binary equivalent of the gray code (1110). 5

OR

P.T.O.



12. a) Simplify the expression using Quine Mc Clusky method.
 $F(w, x, y, z) = \sum m(0, 1, 2, 8, 10, 11, 14, 15)$ 12
- b) Simplify using Boolean algebra.
 $F = w\bar{x} + \bar{y}z + \bar{w}y\bar{z}$ and implement using universal gates. 8

Module – II

13. a) Design a 4 bit full adder with carry look ahead generator. 12
- b) Use a multiplexer having three select input to implement the logic function
 $f = \sum m(0, 1, 4, 10, 11, 14, 15)$. 8
- OR
14. a) With the help of relevant circuit schematics, briefly describe the operation of CMOS NAND and NOR gates. 10
- b) What are the classifications of logic family ? Compare their characteristics. 10

Module – III

15. a) Design and implement a 3 bit synchronous up/down counter using JK flip-flop. 12
- b) With circuit diagram explain 4 bit PIPO shift register. 8
- OR
16. a) Explain the operational basics of binary ripple counters. Implement a 3 bit binary ripple counter using JK flip-flop. 10
- b) Explain 4 bit Johnson counter with waveforms. 10

Module – IV

17. a) Design astable and monostable multivibrators using discrete gates. Explain its working. 12
- b) What is the difference between static and dynamic RAM ? 8
- OR
18. a) Give the advantages of programmable logic devices over fixed logic devices. Explain PAL architecture. 14
- b) Differentiate between ROM and RAM. 6