



(Pages : 2)

A – 4189

Reg. No. : .....

Name : .....

**Fourth Semester B.Tech. Degree Examination, June 2016  
(2013 Scheme)**

**13.405 : POWER ELECTRONICS (E)**

Time : 3 Hours

Max. Marks : 100

**PART – A**

Answer **all** questions :

**(10×2=20 Marks)**

1. What is meant by commutation ?
2. Draw the thermal equivalent circuit of SCR.
3. What is forward voltage triggering ?
4. Draw the characteristics of UJT and GTO.
5. What is the difference in construction of IGBT and power MOSFET ?
6. What is freewheeling diode ?
7. Write condition for inverter operation of converter (RLE load). Draw waveforms.
8. Draw the output waveform of 6 pulse converter.
9. What is overlapping period ?
10. Differentiate between MPWM and SPWM.



**PART – B**

**Module – I**

**(4×20=80 Marks)**

11. a) Explain two transistor analogy of SCR. 10  
b) Discuss the VI characteristics of SCR with relevant waveforms. 10
- OR
12. a) Explain in detail the static and dynamic equalization circuit with necessary expression and derivation. 15  
b) Differentiate between forced commutation and natural commutation. 5

P.T.O.



### Module – II

13. Explain in detail with relevant design equations, the following triggering circuits for a SCR. 20

- i) RC triggering circuit ii) UJT trigger circuit  
 iii) R triggering circuit.

OR

14. a) Describe the construction operation and VI characteristics of a TRIAC. 10

b) Explain the operation and VI characteristics of IGBT and GTO. 10

### Module – III

15. Explain in detail the operation of  $1\phi$  phase controlled converter with RLE load and also derive expression for load current (draw necessary diagrams and waveforms). 20

OR

16. Explain in detail about  $3\phi$  fully controlled bridge converters with working principle and relevant waveforms. 20

### Module – IV

17. With a neat diagram and waveforms, explain voltage commutated chopper and derive necessary expressions. 20

OR

18. i) A single phase full bridge inverter is connected to an RL load. For a dc source voltage of  $V_s$  and output frequency  $f = 1/T$ , obtain expressions for load current as a function of time for the first two half cycles of the output voltages. 10

ii) Derive also the expression for steady state current for the first two half cycles. 4

iii) For  $R = 20\Omega$  and  $L = 0.1\text{ H}$ , obtain current expression for parts

i) and ii) in case source voltage is 240 V dc and frequency of output voltage is 50 Hz. 6