



Reg. No. : .....

Name : .....

**Third Semester B.Tech. Degree Examination, December 2015  
(2008 Scheme)**

**Branch : Electrical and Electronics**

**08.304 : NETWORK ANALYSIS AND SYNTHESIS (E)**

Time : 3 Hours


Max. Marks : 100

Answer **all** questions from Part **A** and **one full** question from **each** Module of Part **B**.


**PART – A**



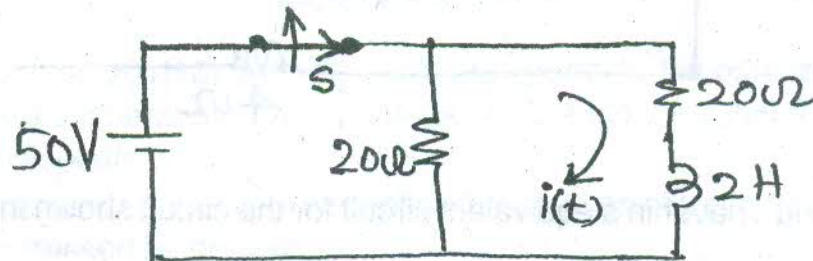1. State and explain Super position theorem.
2. With an example explain node voltage analysis.
3. Determine the resonant frequency for a series circuit consisting of  $10\Omega$ ,  $0.5\text{ mH}$  and  $10\mu\text{F}$ .
4. A  $3-\phi$  balanced delta connected load of  $(4+j8)\Omega$  perphase is connected across a  $400\text{ V}$ ,  $3-\phi$  balanced supply. Calculate the total active power drawn by the load.
5. For the circuit shown in Figure, find the current equation when the switch is opened at  $t = 0$ .



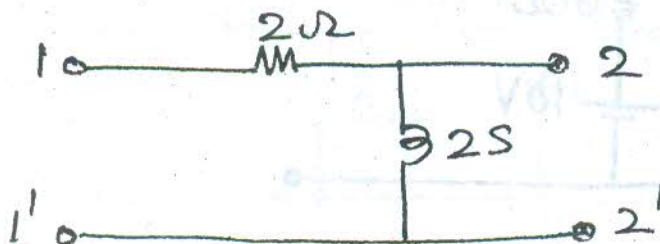6. For the network shown in figure, obtain the transfer functions  $G_{21}(s)$  and  $Z_{21}(s)$ .






7. Explain Y – parameters of a two port network.
8. What are the drawbacks of constant K type filters ?
9. Derive an expression for the characteristic impedance of a symmetrical  $\pi$  –section.
10. Check the positive realness of the following function :  $z(s) = \frac{s+3}{s+1}$

(10×4 = 40 Marks)


## PART – B

## Module – I

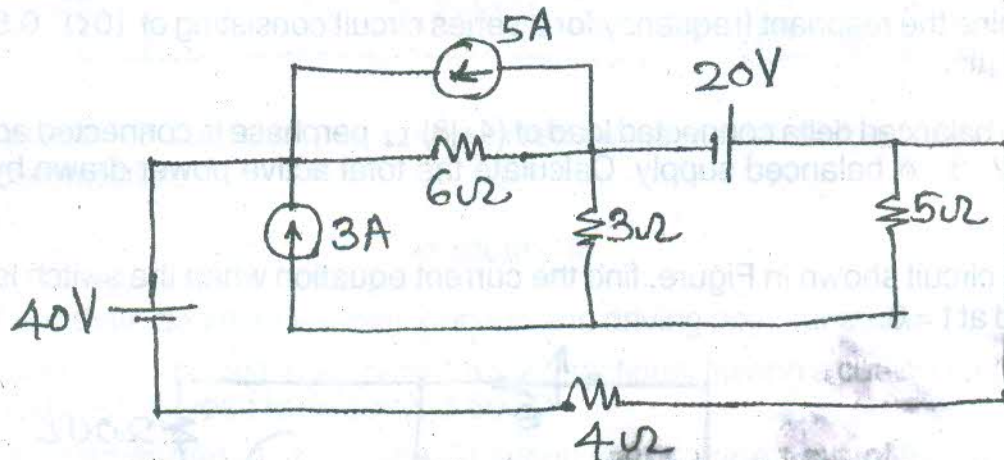11. a) Determine the power dissipated in  $5\Omega$  resistor in the circuit shown in figure. 12



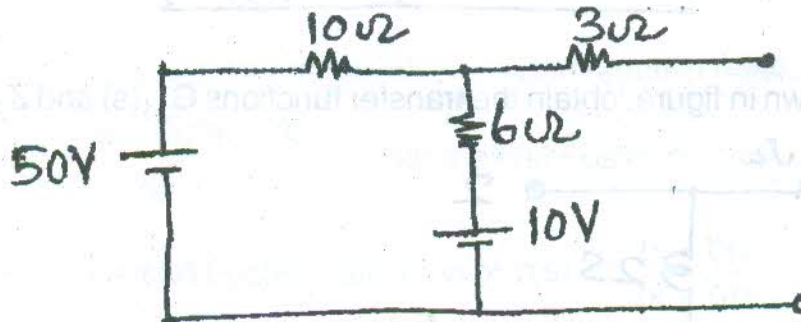- b) Find Thevenin's equivalent circuit for the circuit shown in figure. 8




OR







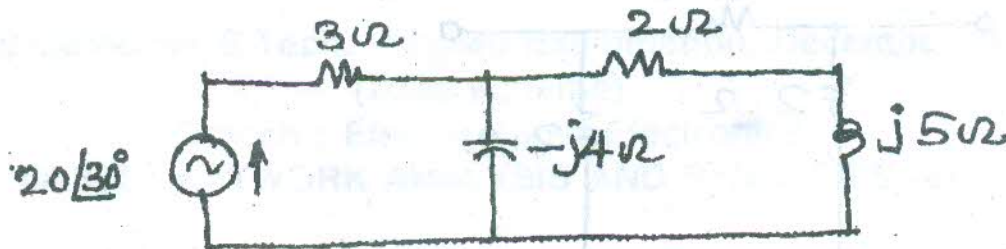12. a) For the circuit shown in figure, determine the power output of the source and the power in each resistor. 6




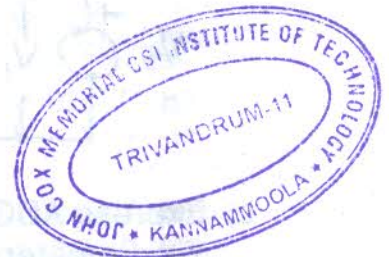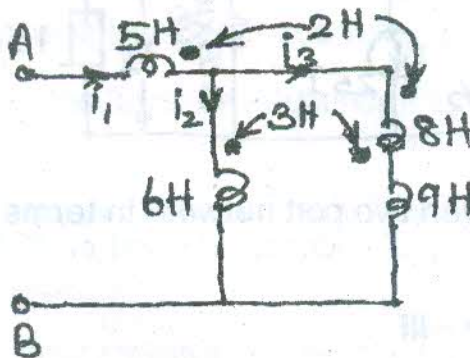- b) A symmetrical 3- $\phi$ , 100 V, 3 wire supply feeds an unbalanced star connected load with impedances of the load as  $5\angle 0^\circ \Omega$ ,  $2\angle 90^\circ \Omega$ , and  $4\angle -90^\circ \Omega$ . Find the line currents. 7
- c) Calculate the effective inductance of the circuit shown in figure across AB. 7



Module - II

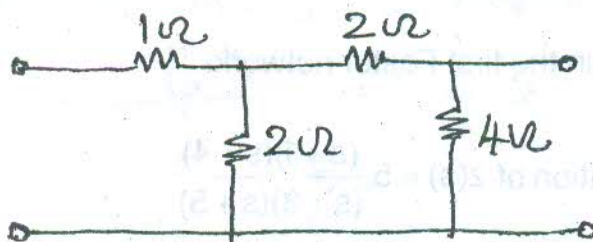
13. a) Two impedances  $(20+j10)$  and  $(10 - j30)$  are connected in parallel and this combination is connected in series with  $(30 + jX)$ . Find the value of X which will produce resonance. 6
- b) Derive expressions for transient current and voltage across inductor in series RL circuit impressed by dc voltage. 7
- c) Find the Y-parameters for the network shown in figure. 7




OR



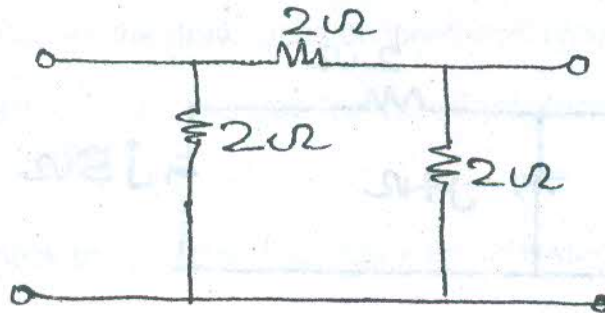14. a) Find the transmission parameters for the circuit shown in figure. 6



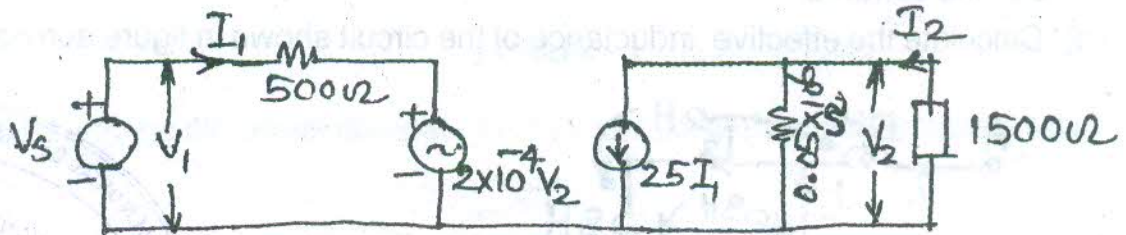- b) For the hybrid equivalent circuit shown in figure, determine the current gain and the voltage gain. 7



- c) Express ABCD parameters of a given two port network in terms of the Y-parameters. 7

### Module – III

15. a) Differentiate between transfer function and driving point function. 6  
 b) Design a K-high pass filter (both T and  $\pi$  sections) having a cut-off frequency of 1 kHz with a load resistance of 600Ω. 7  
 c) Design an m-derived low pass T-section filter having a cut-off frequency of 6 kHz and a design impedance of 500Ω. The frequency of infinite attenuation should be 1.75 times the cut-off frequency. 7

OR

16. a) The driving point impedance of a one-port reactive network is given by

$$z(s) = 5 \frac{(s^2 + 4)(s^2 + 25)}{s(s^2 + 16)}$$

obtain the first Foster network. 7

- b) Find the second Foster realisation of  $z(s) = 5 \frac{(s+1)(s+4)}{(s+3)(s+5)}$ . 7

- c) Find the first Cauer form of the function  $z(s) = \frac{(s+3)(s+7)}{(s+2)(s+4)}$ . 6