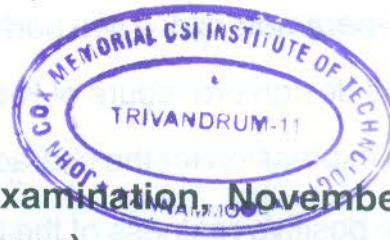


Reg. No. : .....

Name : .....



Third Semester B.Tech. Degree Examination, November 2013  
(2008 Scheme)

Branch : Electrical and Electronics

08.304 : NETWORK ANALYSIS AND SYNTHESIS (E)


Time : 3 Hours

Max. Marks : 100


**Instruction :** Answer **all** questions from Part A and one **full** question from **each** Module of Part B.

## PART - A

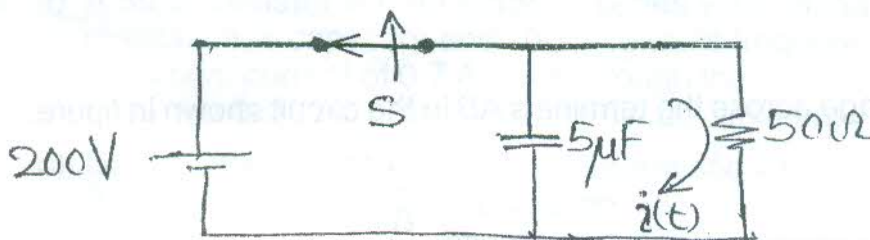1. State and explain Thevenin's theorem.
2. With an example explain mesh current analysis.
3. For a series circuit consisting of  $10 \Omega$ ,  $0.1 \text{ H}$  and  $10 \mu\text{F}$ , determine the impedance at  $10 \text{ Hz}$  above resonant frequency.
4. A balanced delta connected load of  $(2 + j3) \Omega$  per phase is connected to a balanced  $3 - \phi$ ,  $440 \text{ V}$  supply. Find the total active power and reactive power in the circuit.
5. For the circuit shown in figure, find the current equation when the switch is opened at  $t = 0$ .



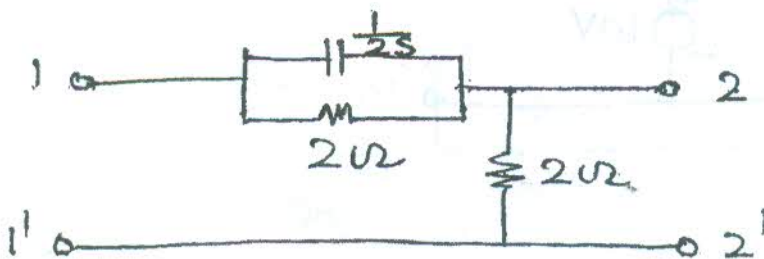6. For the network shown in figure, obtain the transfer functions  $G_{21}(s)$  and  $Z_{21}(s)$ .





7. Explain Z-parameters of a two port network.
8. Outline the design procedure of K-type high pass filter.
9. Derive an expression for the characteristic impedance of a symmetrical T-section.
10. Check the positive realness of the following function :

$$Z(s) = \frac{(s^2 + 2s + 25)}{(s + 4)}$$


(10×4=40 Marks)

PART - B

MODULE - I


11. a) Find the power delivered by the 5A current source in the circuit shown in figure by using nodal method.

10

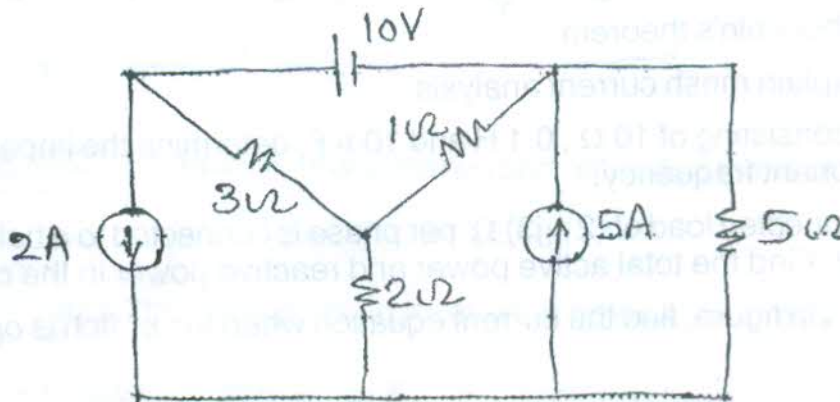

- b) Determine the voltage across the terminals AB in the circuit shown in figure.

10

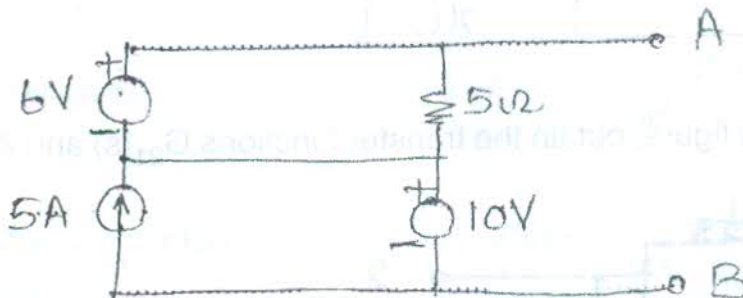


OR



12. a) For the circuit shown in figure, determine the current  $I_L$  by applying Thevenin's theorem.

6

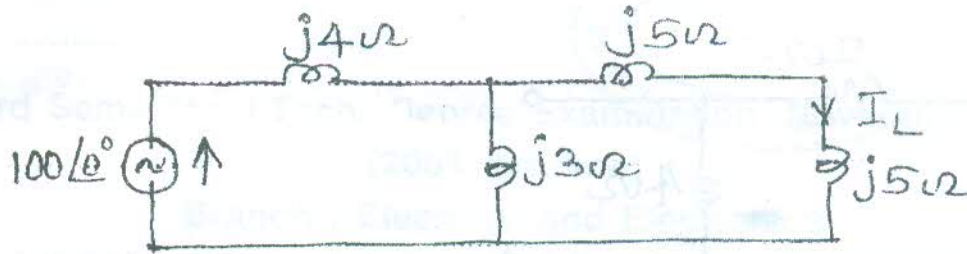


- b) A 3- $\phi$  three wire unbalanced load is star connected. The phase voltages of the two arms are  $V_R = 100 \angle -10^\circ$  and  $V_Y = 150 \angle 100^\circ$ . Calculate voltage between star point of the load and the supply neutral.

7

- c) For the circuit shown in figure, find the ratio  $\frac{V_2}{V_1}$ .

7

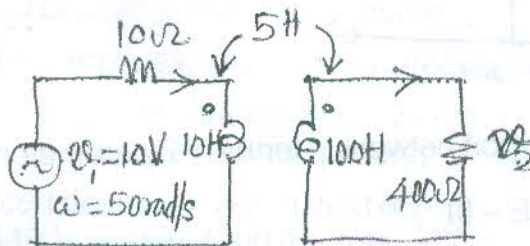

MODULE - II

13. a) A 50  $\Omega$  resistor is connected in series with an inductor having internal resistance, a capacitor and 100 V variable frequency supply. At 200 Hz, a maximum current of 0.7 A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants.


6

- b) Derive expressions for transient current and voltage across capacitor in series RC circuit impressed by dc voltage.

7

- c) Find the transmission parameters for the circuit shown in figure.

7

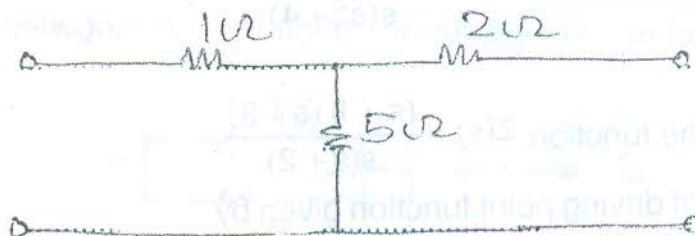


OR




14. a) Find h-parameters for the network shown in figure :

6

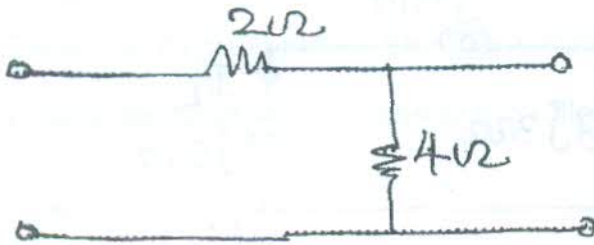

- b) Find the Z-parameters for the circuit shown in figure.

7

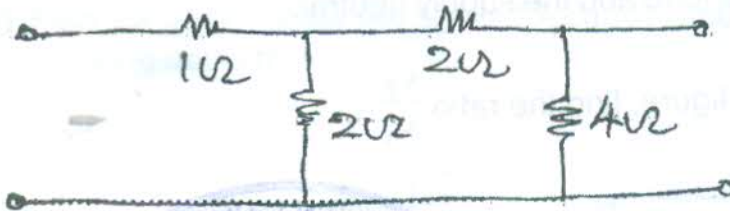

- c) Express ABCD parameters of a given two port network in terms of Z parameters.

7

### MODULE - III

15. a) Discuss about the restrictions on location of poles and zeroes in driving point function. 6
- b) Design a K-low pass filter (both T and  $\pi$  sections) having a cut-off frequency of 2 KHz to operate with a terminated load resistance of 500  $\Omega$ . 7
- c) Design an m-derived  $\pi$ -section low pass filter having cut-off frequency of 1 KHz, design impedance of 400  $\Omega$ , and the resonant frequency 1100 Hz. 7

OR

16. a) Find the second Foster realisation of  $Z(s) = \frac{4(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)}$ . 7

- b) Find the first Foster form of the function  $Z(s) = \frac{(s + 1)(s + 3)}{s(s + 2)}$ . 7

- c) Find the second Cauer form of driving point function given by

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$$

6